

Sri Siddhartha Institute of Technology, Tumkur
(A constituent college of Sri Siddhartha Academy of Higher Education, Tumkur)

22EE102: BASIC ELECTRICAL ENGINEERING

Date: 06/11/23

TEST 1

Time: 60 min

Max Marks: 30

Q.No		Marks	CO	BL
1.	Define R.M.S value and deduce the relation between R.M.S value and Max Value.	6	1	1,3
2.	Examine whether the current in pure inductor lags the applied voltage by 90° .	6	1	3
3.	Demonstrate that the average power in pure inductor is zero.	6	1	3
4.	A pure inductance of 300mH is connected in series with a pure resistance of $100\ \Omega$. The circuit is supplied from 250V, 50Hz source. Evaluate the power factor and power consumed in the circuit.	6	1	3,4
5.	List the advantages of three phase system over single phase system	6	2	2

Sri Siddhartha Institute of Technology, Tumkur

(A constituent college of Sri Siddhartha Academy of Higher Education, Tumkur)

22EE102: BASIC ELECTRICAL ENGINEERING

Date: 11/12/23

CIE-2

Max Marks: 30

Time: 60 min

Q.No		Marks	CO	BL
1.	A balanced star connected load of $(8 + j6) \Omega$ per phase are connected to a three phase 400 V supply. Evaluate the line current, power factor, power, reactive volt ampere.	6	2	3
2.	Examine whether, two wattmeter are sufficient to measure three phase power. <i>using star connection</i>	6	2	3
3.	Three similar choke coils each having resistance 10Ω and reactance 10Ω are connected in star across a 440 V, three phase supply. Evaluate the current and the reading of each of two wattmeters connected to measure power.	6	2	3,4
4.	With a neat sketch explain pipe earthing	6	3	2
5.	Derive EMF equation of transformer.	6	4	3

Common for sections: H,I, J,K, L, M, N

Sri Siddhartha Institute of Technology, Tumkur

(A constituent college of Sri Siddhartha Academy of Higher Education, Tumkur)

22EE102: BASIC ELECTRICAL ENGINEERING

Date: 04/01/24

CIE3

Max Marks: 20

Time: 60 min

Q.No		Marks	CO	BL
1.	With neat sketch, explain the construction of DC machine.	8	4	2
2.	Derive an expression for armature torque of DC motor.	6	4	3
3.	A 250KVA, 11000/415 V, 50Hz single phase transformer has 80 turns on the secondary. Evaluate i) rated primary and secondary currents ii) number of primary turns iii) maximum value of flux.	6	4	4

Common for sections: H, I, J, K, L, M, N



SRI SIDDHARTHA ACADEMY OF HIGHER EDUCATION TUMAKURU
(Deemed to be University), Accredited 'A+' Grade by NAAC.

SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY- TUMAKURU
(A Constituent College of Sri Siddhartha Academy of Higher Education, Tumakuru)

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING
Accredited by NBA, New Delhi in Tier 1 for 3 years (2023-2026)

22EE202: BASIC ELECTRICAL ENGINEERING

Max. Marks: 30

Date: 01.04.2024

CIE-I


Duration: 60

Answer all the questions:

Q. No.	Questions	M	CO	BL	PO
1	Define i) Real Power ii) Apparent Power iii) Reactive Power.	06	01	01	01
2	With the help of circuit diagram and phasor diagram, discuss the behavior of R-C series circuit.	06	01	02	01
3	A parallel circuit comprises of a resistor of 10Ω in series with an inductor of $0.12H$ in one branch and a resistor of 20Ω in series with a capacitor of $40\mu F$ in another branch connected across $200V$, $50Hz$ supply. Evaluate i) current in each branch ii) supply current iii) total power. Sketch the phasor diagram.	06	01	04	02
4	A non- inductive resistor of 10Ω is in series with a capacitor of $100\mu F$ across a $250V$, $50Hz$ AC supply. Evaluate the current taken by the capacitor and power factor of the circuit.	06	01	04	02
5	Develop the relationship between line and phase values of current and voltage in a three phase balanced star connected system.	06	02	02	02

Legend:

M – Marks, CO – Course Outcome, BL – Bloom's Level, PO – Program Outcome, PSO – Program Specific Outcome

 **SRI SIDDHARTHA ACADEMY OF HIGHER EDUCATION TUMAKURU**
(Deemed to be University), Accredited 'A+' Grade by NAAC.

SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY- TUMAKURU
(A Constituent College of Sri Siddhartha Academy of Higher Education, Tumakuru)

DEPARTMENT OF ELECTRICAL AND ELECTRONICS ENGINEERING
Accredited by NBA, New Delhi in Tier I for 3 Years (2023-2026)

22EE202: BASIC ELECTRICAL ENGINEERING

CIE-3

Max. Marks: 20

Duration: 60 minutes

Date: 03.06.2024

Answer all the questions:

Q. No.	Questions	M	CO	BL	PO
1.	Explain the construction of DC machine with a neat sketch.	08	04	02	01
2.	Explain the various losses in a transformer.	06	03	02	01
3.	A 200V DC series motor is taking a current of 40A. Resistance of armature is 0.5Ω and resistance of series field is 0.25Ω . Evaluate the back emf.	06	04	04	02



SRI SIDDHARTHA ACADEMY OF HIGHER EDUCATION TUMAKURU
(Deemed to be University), Accredited A⁺ Grade by NAAC.



SRI SIDDHARTHA INSTITUTE OF TECHNOLOGY- TUMAKURU
(A constituent College of Siddhartha Academy of Higher Education, Tumakuru)

B.E., SEMESTER END EXAMINATION JAN - FEB 2024

22EE102 : BASIC ELECTRICAL ENGINEERING

TIME: 3.00 Hrs

SEM: I

MAX MARKS: 100

NOTE: Answer any five full questions selecting one full question from each choice.

	M	CO	BL
1.a) Discuss Average value of an alternating quantity and derive the relation with maximum value.	6	1	3
b) Examine whether the current in pure capacitor leads the applied voltage by 90°.	7	1	3
c) Two impedances $Z_1 = (10+j15) \Omega$ and $Z_2 = (5 - j8) \Omega$ are connected in parallel across a voltage source. If the total current drawn is 10 A, evaluate the currents in Z_1 and Z_2 and power factor of the circuit.	7	1	3
OR			
2.a) Sketch the sinusoidal alternating current waveform and define the following terms (i) instantaneous value(ii) amplitude (iii) cycle(iv) time period (v) frequency.	6	1	2
b) Examine whether the current in pure capacitor leads the applied voltage by 90°.	7	1	3
c) An e.m.f whose instantaneous value is $100 \sin(314t - \pi/4)$ volts is applied to a circuit and the current through it is $20 \sin(314t - \pi/2)$ Amperes. Evaluate the frequency and the values of circuit elements, assuming a series combination.	7	1	4
3.a) Develop the relationship between line and phase values of current in a three phase balanced star connected system.	6	2	3
b) With the help of a neat sketch and truth table explain two and three way control of lamp.	8	3	2
c) A star connected inductive load takes 8 kW at 0.8 pf lag, when connected to 460 V, 3-phase supply. Calculate the readings of two wattmeter to measure power.	6	2	1
OR			
4.a) Develop the relationship between line and phase values of current in a three phase balanced star connected system.	7	2	
b) Two wattmeter are used to measure power consumed in a delta connected load. Each branch of load is having impedances of 20Ω at an angle 60° . Supply voltage is 400V. Calculate the power and readings of individual wattmeter.	7	2	
c) With the help of a neat sketch, explain pipe earthing.	6	3	
5.a) Explain the various losses in a transformer.	6	2	
b) A 250 kVA, 11000/415 V, 50Hz single phase transformer has 80 turns on the secondary. Evaluate (i) rated primary and secondary currents(ii) number of primary turns (iii) maximum value of flux.	6	4	